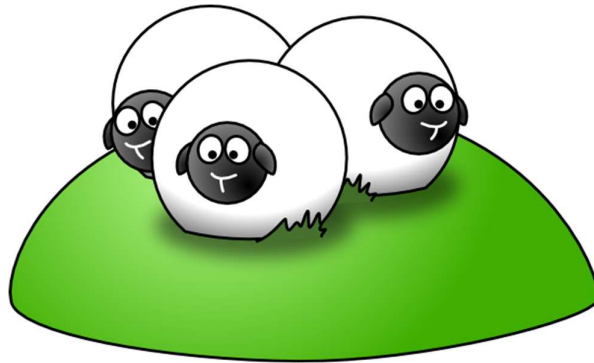


Farmer Giles' Lost Sheep Circuit

Silver Task



All the sheep from belonging to Farmer Giles have escaped from his farm to a nearby hillside, where they have joined other sheep. He wishes to recover all his sheep and knows the following:

- NOT one of his sheep is black as he believes these to be unlucky.
- AND all his sheep are branded 'G', OR have a collar

Using the following:

B = black sheep

G = branded 'G'

C = has a collar

F = belongs to Farmer Giles

- Draw a truth table from these conditions to show those sheep owned by Farmer Giles.
- From your table produce a Boolean expression to represent those sheep owned by Farmer Giles
- Build a logic circuit on logic.ly that is capable of carrying out the expression. Screen shot the final circuit.



Truth Table

B	G	C	F

Boolean Algebra

Circuit